

**Contents**

March 2011

<b>1.0 Introduction .....</b>	<b>1</b>
<b>2.0 Closed Circuit TV Application .....</b>	<b>3</b>
<b>3.0 Industrial Application .....</b>	<b>5</b>
<b>4.0 Musical Studio Applications .....</b>	<b>6</b>
4.1 Audio Mixer Circuit Operation.....	6
4.2 Programmable Attenuator Circuit Operation ..	7

**1.0 Introduction**

Like all monolithic analog switches, the Zarlink MT88xx family of analog switches exhibits resistive characteristics when turned on. Most applications will not be adversely affected by the ON resistance or its variations with these parameters. In some systems and applications with more stringent specifications, special considerations may be required. In cases such as driving through the switches into low impedance loads, or using the device in a gain control circuit, it becomes necessary to consider the switch resistance in design equation.

Other Zarlink analog switches characteristics can be summarized as follows;

- Transparent and bi-directional switch with low on resistance
- Capable of passing analog signal, digital signal and DC voltage
- 12Vp-p analog signal capability
- DC to 45 MHz bandwidth
- Full CMOS switch for low distortion
- Wide operating voltage range from 4.5 V to 13.5 V

Traditionally, Zarlink analog switches have been used primary in Telecom applications. However, the unique characteristic mentioned above also makes Zarlink analog switches suitable for a wide variety of applications as follows.

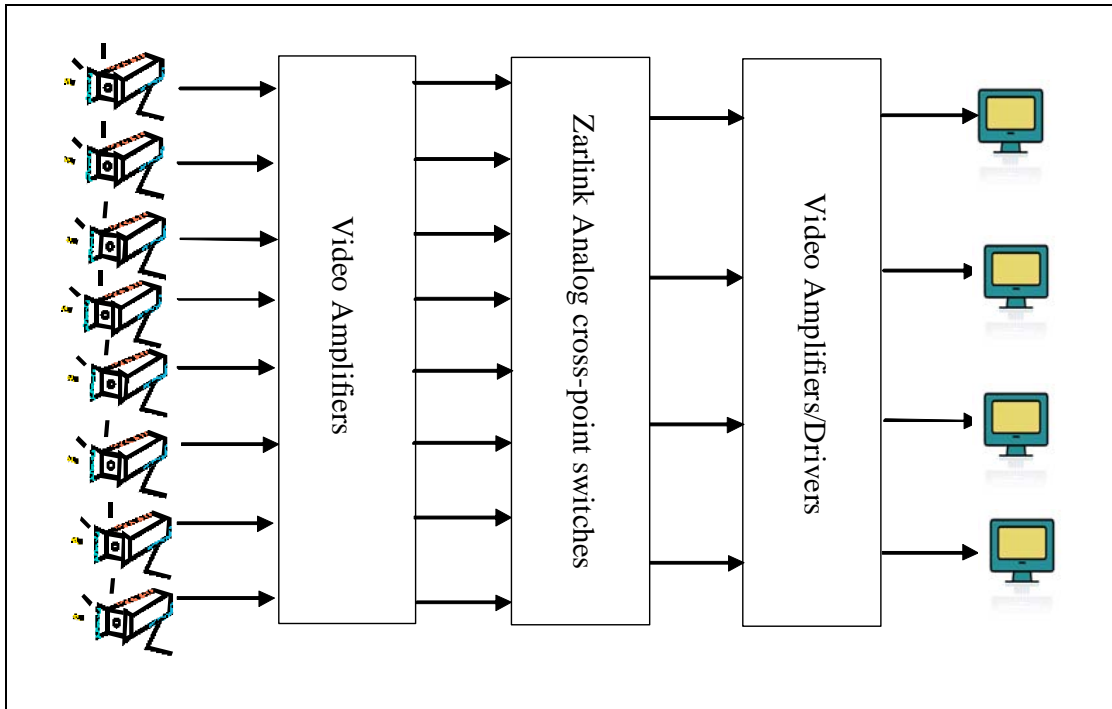


Figure 1 - Typical Video Surveillance Systems

## 2.0 Closed Circuit TV Application

Figure 1 shows a typical closed circuit TV system using Zarlink analog cross-point switches. Analog cross-point switches allow multiple video sources switched to multiple output devices, e.g., video monitor, video recorder etc. External video amplifiers are required as the input buffers and output buffers to drive the video loads.

The reference design shown in Figure 2 utilizes the CLC2005, CADEKA dual channel video amplifier, and the MT8816, Zarlink 8 x 16 analog switch array. Both operate from a single 5 V supply providing a significant competitive advantage versus many  $\pm 5$  V solutions used today. The CLC2005 is used to buffer the inputs of the MT8816 and to provide gain and drive capability for each MT8816 output. Each channel of the CLC2005 can drive 3 video loads allowing for increased system capability. The MT8816 offers designers ease-of-use and flexibility by providing 16 inputs that can be switched to any of the 8 outputs or 8 inputs that can be switched to any of the 16 outputs.

The reference design provides video surveillance system designers a low cost solution with performance that exceeds the requirements of standard definition video. For full scale video, the reference design offers -0.3 dB bandwidth of 4 MHz, -1 dB bandwidth of 10 MHz, -3 dB bandwidth of 35 MHz, differential gain/phase of 0.16%/0.33°, and signal-to-noise ratio better than 90 dB. A FT245R USB FIFO from Future Technology Devices International (FTDI) provides a standard USB interface for a PC. Through this USB connection the PC controls the programming of the switching system.

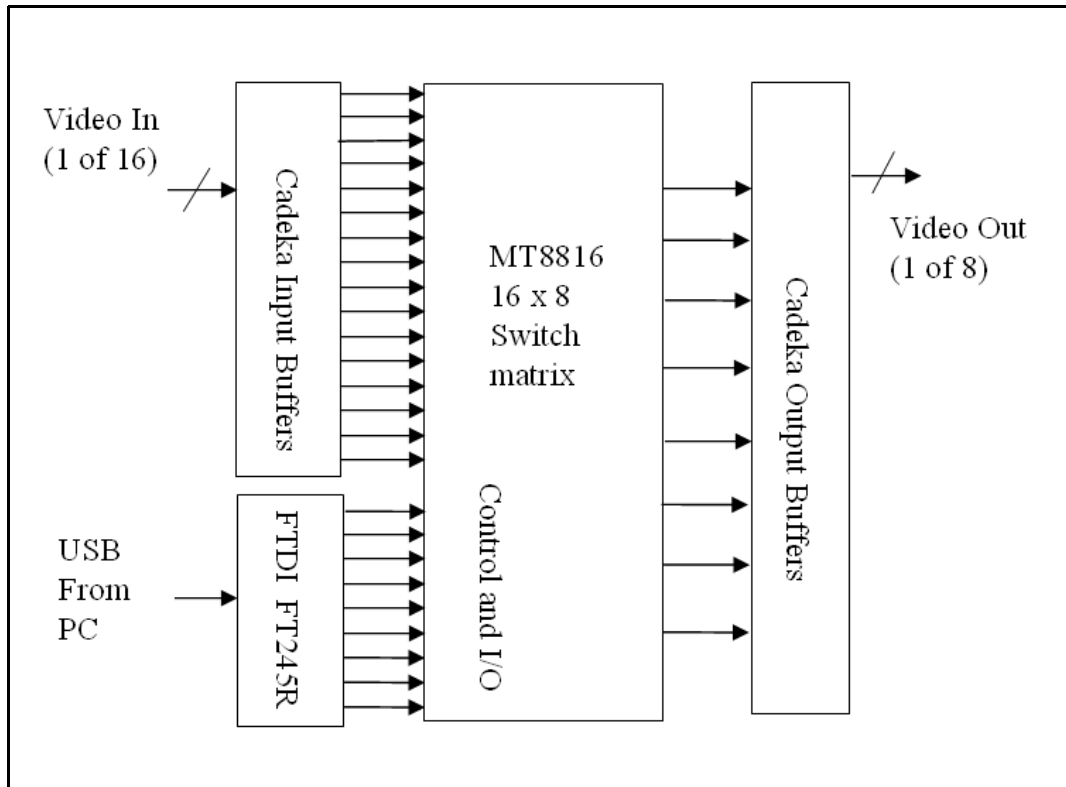


Figure 2 - Block Diagram of a 16 x 8 Video Switch Matrix



### 3.0 Industrial Application

Figure 4 shows a typical application of the MT8816 in a factory environment where the MT8816 could be used in a remote control room. Basically, part of the MT8816 switch array is used to support a closed circuit TV system. Cameras should be installed in all locations where human access is limited. Other part of the MT8816 could be used to connect up certain system test points to different electronic measurement equipment. For example, the system test points could be part of the furnace of the smelter where temperature, electrical operation detail could be connected to the thermometer, voltmeter or oscilloscope of the remote control panel. When abnormal conditions are detected, the remote control panel would then connect control voltages to the factory floor, e.g., shutting down the furnace that display elevated temperature, and also turn the alarm on.

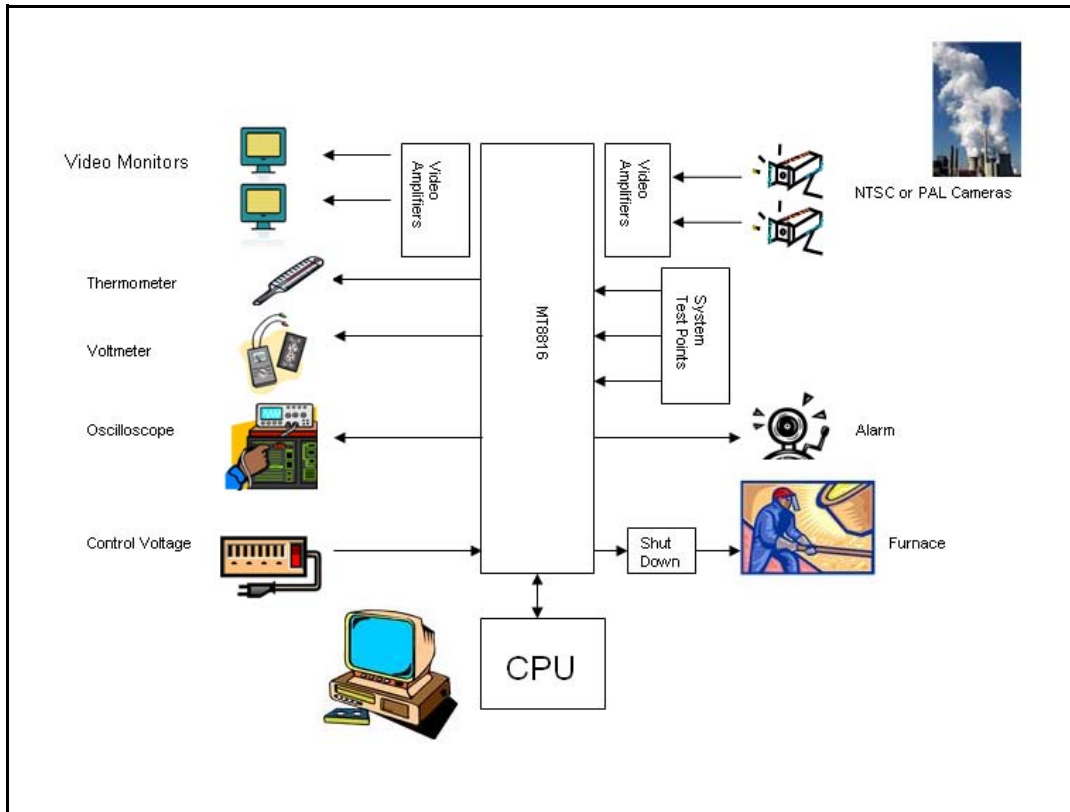


Figure 4 - A Steel Mills Remote Monitor/Control System

### 4.0 Musical Studio Applications

#### 4.1 Audio Mixer Circuit Operation

A simple dual mixer is shown in Figure 5. Eight different audio sources are connected at the inputs Y0 to Y7. Outputs X0 to X4 are connected to operational amplifier x3 as a four inputs summing amplifier. Outputs X4 to X7 are connected to operational amplifier x4 as another 4 inputs summing amplifier. A micro-controller is used to select any 4 of audio inputs for the mixers. To reduce gain error due to the switch ON resistance, 100 K ohms are used for gain setting.

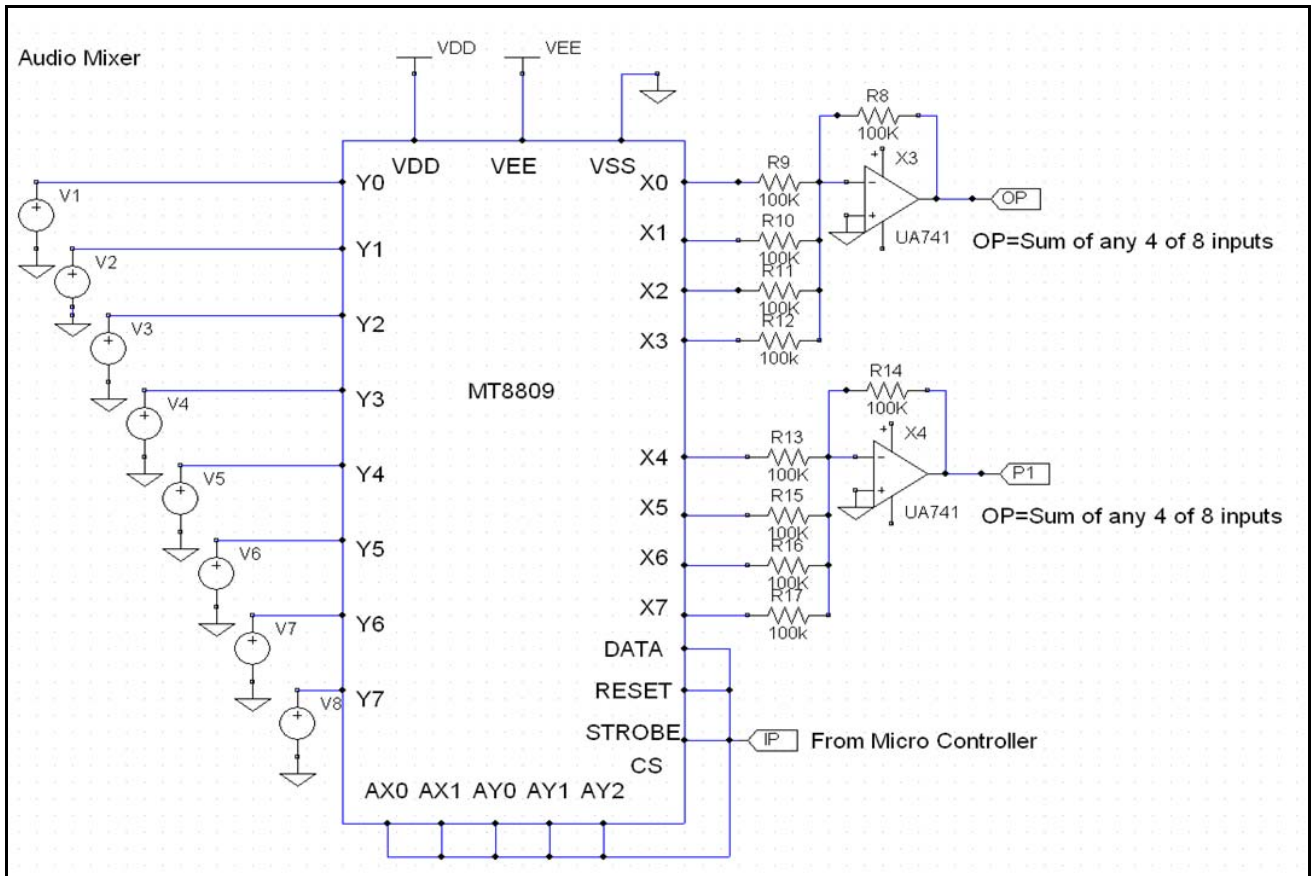


Figure 5 - Audio Mixer

### 4.2 Programmable Attenuator Circuit Operation

The programmable attenuator shown in Figure 6 is capable of providing up to -61 dB of attenuation or 20 dB of gain. Selecting the input attenuation is accomplished via the address inputs AY0, AY1, and AY2 and can be chosen in 3 dB step. Selecting the output gain is accomplished by the address inputs AX0 and AX1. The range is selected in 20 dB steps by connecting an attenuated input signal (Y0 to Y7) onto the appropriate outputs (X0 to X3). The attenuated input signal is buffered after passing through the switch to eliminate the gain error introduced by the ON resistance and also provide low output impedance to the summing amplifier X3.

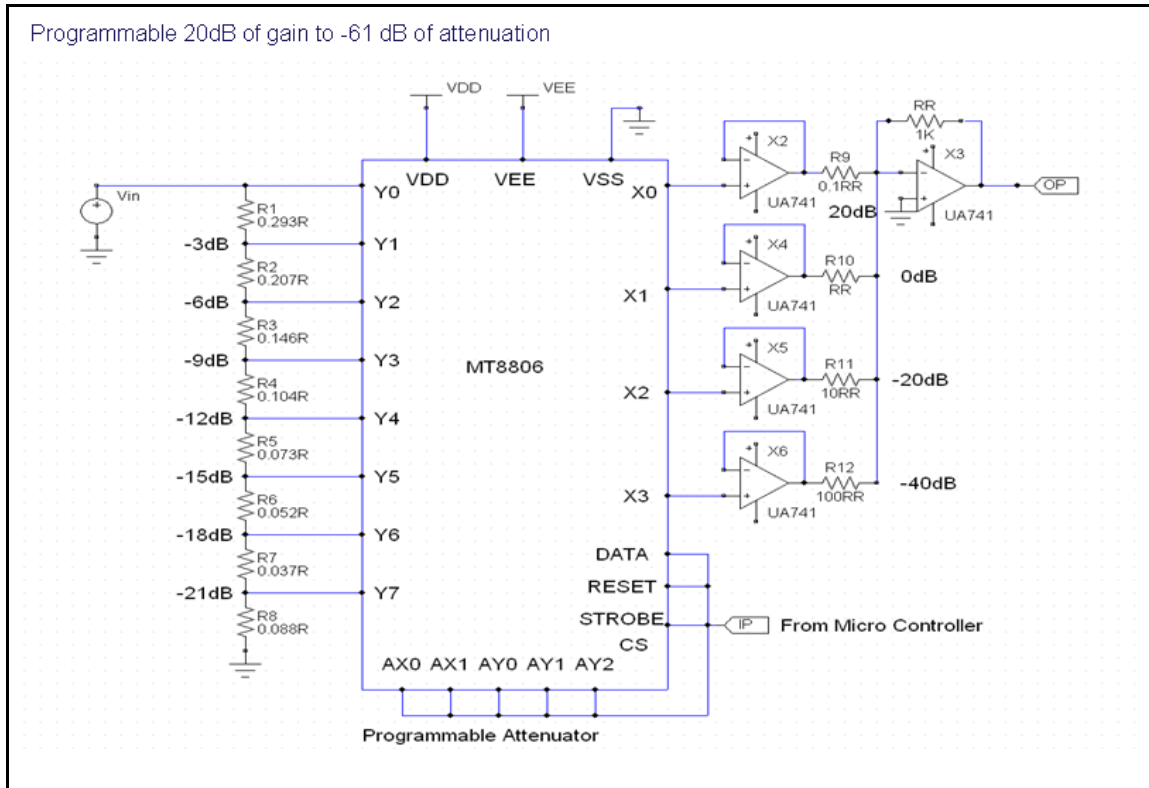


Figure 6 - Programmable Gain/Attenuation



**For more information about all Zarlink products  
visit our Web Site at  
[www.zarlink.com](http://www.zarlink.com)**

Information relating to products and services furnished herein by Zarlink Semiconductor Inc. or its subsidiaries (collectively "Zarlink") is believed to be reliable. However, Zarlink assumes no liability for errors that may appear in this publication, or for liability otherwise arising from the application or use of any such information, product or service or for any infringement of patents or other intellectual property rights owned by third parties which may result from such application or use. Neither the supply of such information or purchase of product or service conveys any license, either express or implied, under patents or other intellectual property rights owned by Zarlink or licensed from third parties by Zarlink, whatsoever. Purchasers of products are also hereby notified that the use of product in certain ways or in combination with Zarlink, or non-Zarlink furnished goods or services may infringe patents or other intellectual property rights owned by Zarlink.

This publication is issued to provide information only and (unless agreed by Zarlink in writing) may not be used, applied or reproduced for any purpose nor form part of any order or contract nor to be regarded as a representation relating to the products or services concerned. The products, their specifications, services and other information appearing in this publication are subject to change by Zarlink without notice. No warranty or guarantee express or implied is made regarding the capability, performance or suitability of any product or service. Information concerning possible methods of use is provided as a guide only and does not constitute any guarantee that such methods of use will be satisfactory in a specific piece of equipment. It is the user's responsibility to fully determine the performance and suitability of any equipment using such information and to ensure that any publication or data used is up to date and has not been superseded. Manufacturing does not necessarily include testing of all functions or parameters. These products are not suitable for use in any medical products whose failure to perform may result in significant injury or death to the user. All products and materials are sold and services provided subject to Zarlink's conditions of sale which are available on request.

Purchase of Zarlink's I2C components conveys a license under the Philips I2C Patent rights to use these components in an I2C System, provided that the system conforms to the I2C Standard Specification as defined by Philips.

Zarlink, ZL, the Zarlink Semiconductor logo and the Legerity logo and combinations thereof, VoiceEdge, VoicePort, SLAC, ISLIC, ISLAC and VoicePath are trademarks of Zarlink Semiconductor Inc.

**TECHNICAL DOCUMENTATION - NOT FOR RESALE**

---