

Contents

August 2003

1.0 Summary

2.0 SONET/SDH Linecard Solutions

- 2.1 SONET/SDH Linecard requirements
- 2.2 MT90401 + ZL30406 Solution
 - 2.2.1 Introduction
 - 2.2.2 Design Considerations
 - 2.2.2.1 Device Control and Setup
 - 2.2.2.2 ZL30406 loop filter
 - 2.2.2.3 MT90401 master oscillator selection
 - 2.2.2.4 Power supply decoupling recommendations
 - 2.2.2.5 Clock termination
 - 2.2.3 Jitter Performance

1.0 Summary

This application will provide details on how to combine Zarlink's Digital PLL products with Zarlink's ZL30406 SONET/SDH Clock Multiplier Analog PLL to provide a robust, ultra-low jitter timing solution for SONET and SDH linecards applications. The DPLL will provide important features such as "hitless" reference switching, short term holdover, and rate conversion from low frequency backplane clocks such as 8kHz. The APLL will provide frequency multiplication with ultra-low jitter output clocks that surpass the jitter requirements of Telecordia GR-253-CORE and ITU-T G.813 specifications for rates up to and including OC-48 and STM-16.

Appendix - Reference Schematic

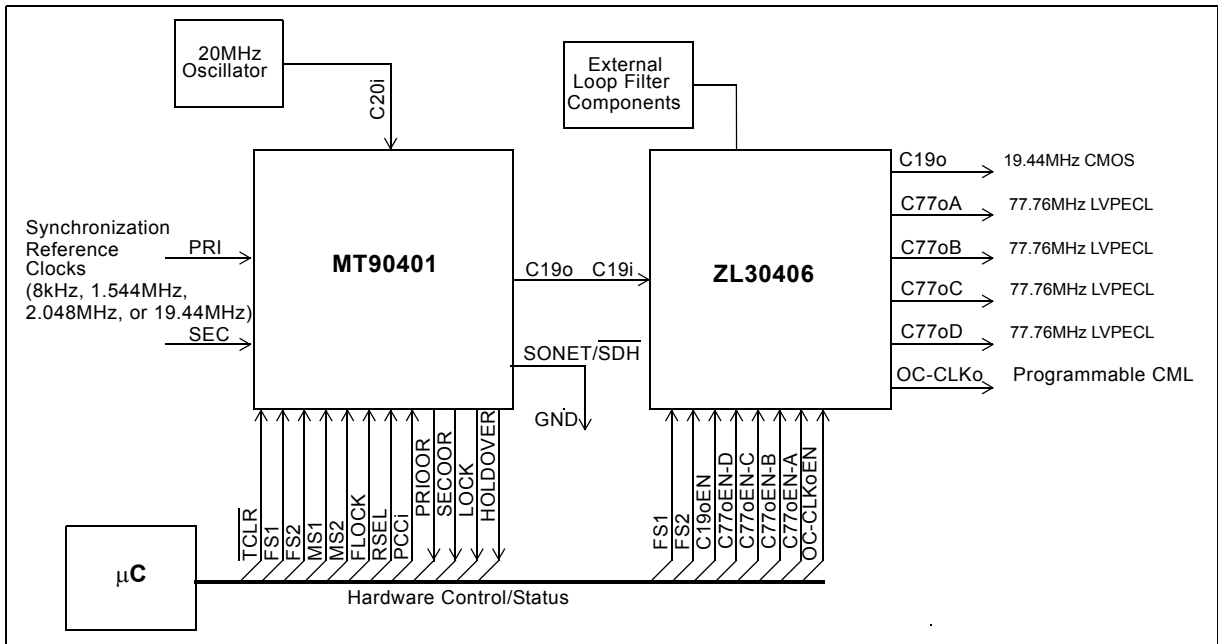


Figure 1 - SONET/SDH Timing Linecard Block Diagram

2.0 SONET/SDH Linecard Solutions

2.1 SONET/SDH Linecard requirements

In most SONET/SDH clock architectures, the central timing cards (Master and Slave) are responsible for much of the system level timing requirements specified by the relevant SONET/SDH standards (Telecordia GR-1244-CORE and GR-253-CORE for SONET and ITU-T G.813 for SDH). The Linecards in these systems are generally responsible for:

- Providing “hitless Reference Switching” between the input references of the Master and Slave timing cards
- Providing low-jitter clocks that comply with the appropriate requirements

Table 1 lists the output jitter generation requirements for SONET (GR-253-CORE) and SDH (G.813 Option 2).

OC-N/STM-N Level	OC-N/STM-N Level	Jitter Measurement Filter	Jitter Requirement (UI)	Jitter Requirement (psec)
OC-3/STM-1	155.52Mbits/sec	12kHz to 1.3MHz	0.1 UIpp	643
			0.01UI _{RMS}	64.3
OC-12/STM-4	622.08Mbits/sec	12kHz to 5MHz	0.1 UIpp	161
			0.01UI _{RMS}	16.1
OC-48/STM-16	2488.32Mbits/sec	12kHz to 20MHz	0.1 UIpp	40
			0.01UI _{RMS}	4

Table 1 - SONET/SDH Jitter Requirements

Table 2 lists the output jitter generation requirements for SDH (G.813 Option 1).

	Interface	Jitter Measurement Filter	Jitter Requirement (UI)	Jitter Requirement (psec)
STM-1	155.52Mbits/sec	1 MHz to 20 MHz	0.1 UIpp	643
		5 kHz to 20 MHz	0.5 UIpp	3215
STM-4	622.08Mbits/sec	250 kHz to 5 MHz	0.1 UIpp	161
		1 kHz to 5 MHz	0.5 UIpp	804
STM-16	2488.32Mbits/sec	65 kHz to 1.3 MHz	0.1 UIpp	40
		500 Hz to 1.3 MHz	0.5 UIpp	200

Table 2 - SDH Jitter Requirements

2.2 MT90401 + ZL30406 Solution

2.2.1 Introduction

Using the MT90401 DPLL(digital phase-locked) with the ZL30406 APLL (analog phase locked-loop) as shown in Figure 1. Zarlink can provide a cost-effective, ultra-low jitter linecard solution for SONET/SDH applications for up to and including OC-48/STM-16 rates.

MT90401 Features:

- “Hitless” reference switching
- rate conversion from low frequency backplane clocks (i.e. 8kHz)
- 1.1Hz loop filter
- Lock indication
- Short term holdover and holdover indication
- Primary and Secondary out of range indications (requires +/-4.6ppm oscillator, see section 2.2.2.3)

ZL30406 features:

- Externally programmable loop filter
- 4 low-jitter 77.76MHz LVPECL output clocks
- 1 low-jitter 19.44MHz CMOS output clock
- 1 low-jitter selectable CML output clock (19.44MHz, 38.88MHz, 77.76MHz, 155.52MHz)

2.2.2 Design Considerations

2.2.2.1 Device Control and Setup

The ZL30406 is easily controlled and monitored through a set of hardware pins. The MT90401 has the option to be controlled via a set of hardware pins or via an 8 bit microprocessor interface. Note, for linecard applications it is recommended that the loop filter of the MT90401 always be set to 1.1Hz (SDH mode) even for SONET applications since the central timing cards will be responsible for the 0.1Hz wander filtering SONET requirement. Please refer to the specific data sheets for detailed information on their operation.

2.2.2.2 ZL30406 loop filter

The characteristics of the ZL30406 Loop filter can be defined by equation 1 and 2, shown below:

Equation 1

$$\text{BANDWIDTH} = \frac{R1 \cdot K}{2\pi}$$

Equation 2

$$\text{DampingFactor} = \zeta = \frac{R1}{2} \cdot \sqrt{K \cdot C1}$$

where,

$$K = \frac{K_{VCO} \cdot I_{CP}}{N} = 11.0625$$

K_{VCO} = VCO gain

I_{CP} = Charge Pump Current

N = Divider Ratio

R1, C1 and C2 = External Loop filter components

From equations 1 and 2, we can develop equations for selecting our Loop filter components for our desired loop bandwidth and damping factor. Note, the damping factor must be greater than 0.707 to ensure that the PLL remains stable.

Equation 3

$$R1 = \frac{2\pi \cdot BW}{K}$$

Equation 4

$$C1 = \frac{\left(\frac{2 \cdot \zeta}{R1}\right)^2}{K}$$

Capacitor C2, is optional, and will not have a large impact on PLL performance, but in general the figure of merit for PLL stability is for C2 to be less than 1/10th the value of C1, employing higher multiples will further improve device stability

When using the MT9046 as the input reference to the ZL30406 the recommended loop filter is shown below.

 


Figure 2 - Recommended Loop Filter

2.2.2.3 MT90401 master oscillator selection

In linecard applications where the SONET/SDH system level timing requirements are met on the master/slave timing cards and there is no requirement for holdover, there is no requirement for a high accuracy, temperature compensated crystal oscillator such as a TCXO or OCXO. A low-cost +/-32ppm (or better) crystal oscillator can be used, except in the following cases:

- If long term (> a few seconds) holdover is required on the linecard
- For the Prior and Secoor status pins of the MT90401 to work properly, a +/-4.6ppm oscillator is required.

2.2.2.4 Power supply decoupling recommendations

Here is a list of power supply recommendations to help ensure optimal jitter performance of the ZL30406 (for more detail please refer to the reference schematic in the appendix of this document):

- Ferrite bead power supply filters should be used to filter high frequency noise from possible onboard digital switching circuit sources.
- Separate nets are recommended to provide some isolation between different power pin groups on the ZL30406 (see VCC_406A and VCC_406B in the reference schematic)
 - For each power net, a small local copper area or “island” should be laid out on an internal layer beneath the applicable ZL30406 power pins.
 - A low pass filter should be placed at the entry to the VCC1 power net.
- A decoupling capacitor should be placed within 200mils of each power pin, on the same side, at the periphery of the TQFP-64 package. The recommended cap value is 0.1uF, size 0603, or 0402.
- Each decoupling capacitor should have separate power and ground vias. Large diameter or double vias are preferred to control inductance.
- For ZL30406 ground pins, use double vias or large diameter vias to connect to the internal ground plane and in general, try to minimize trace and via inductance.
- The ZL30406 BIAS pin is powered from VCC1 through a network of two 33uF caps and a 220 ohm resistor. In layout, these should be grouped close to the BIAS pin and routed with wide traces.

2.2.2.5 Clock termination

Figure 3 through 6 shows some standard termination methods for LVPECL and CML output clocks.

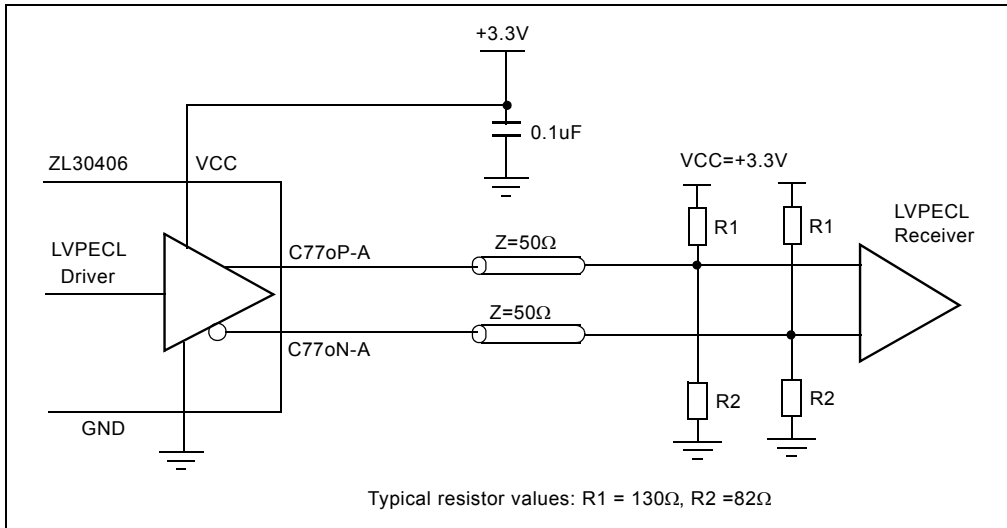


Figure 3 - LVPECL to LVPECL Interface

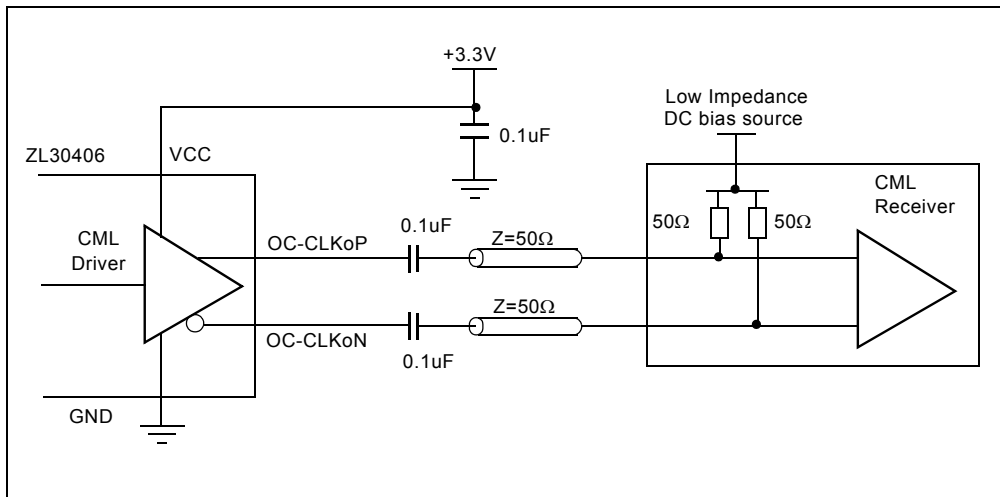


Figure 4 - CML to CML interface

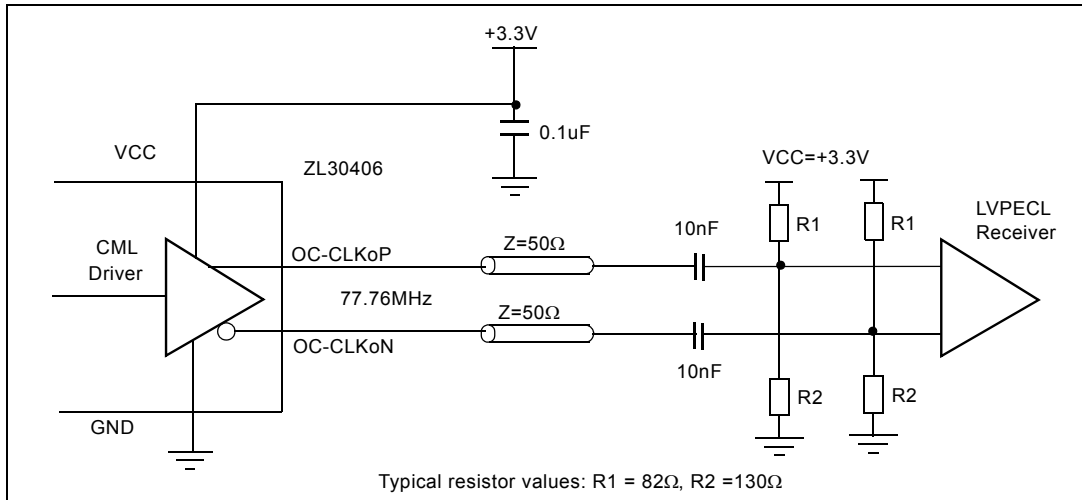


Figure 5 - CML to LVPECL interface

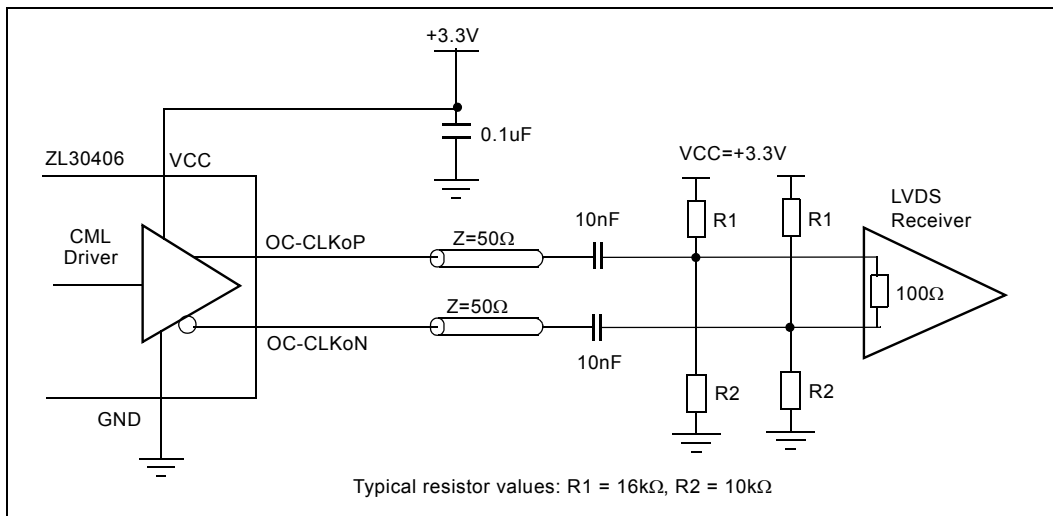



Figure 6 - CML to LVDS interface

2.2.3 Jitter Performance

Table 3 shows typical jitter performance of the MT90401 and ZL30406 versus the output jitter generation requirements of SONET (GR-253-CORE) and SDH (G.813 Option 2).

Jitter Filter	Requirement	155.52MHz CML Output	77.76MHz LVPECL Output	19.44MHz CMOS Output
OC-3/STM-1 (12kHz-1.3MHz)	643ps (pk-pk)	11.59ps (pk-pk)	16.38ps (pk-pk)	27.05ps (pk-pk)
	64.3ps (rms)	0.91ps (rms)	1.29ps (rms)	2.14ps (rms)
OC-12/STM-4 (12kHz-5MHz)	161ps (pk-pk)	15.37ps (pk-pk)	20.70ps (pk-pk)	33.66ps (pk-pk)
	16.1ps (rms)	1.21ps (rms)	1.63ps (rms)	2.65ps (rms)
OC-48/STM-16 (12kHz - 20MHz)	40ps (pk-pk)	17.91ps (pk-pk)	25.02ps (pk-pk)	N/A
	4ps (rms)	1.41ps (rms)	1.97ps (rms)	N/A

Table 3 - Typical jitter performance of the MT90401 + ZL30406

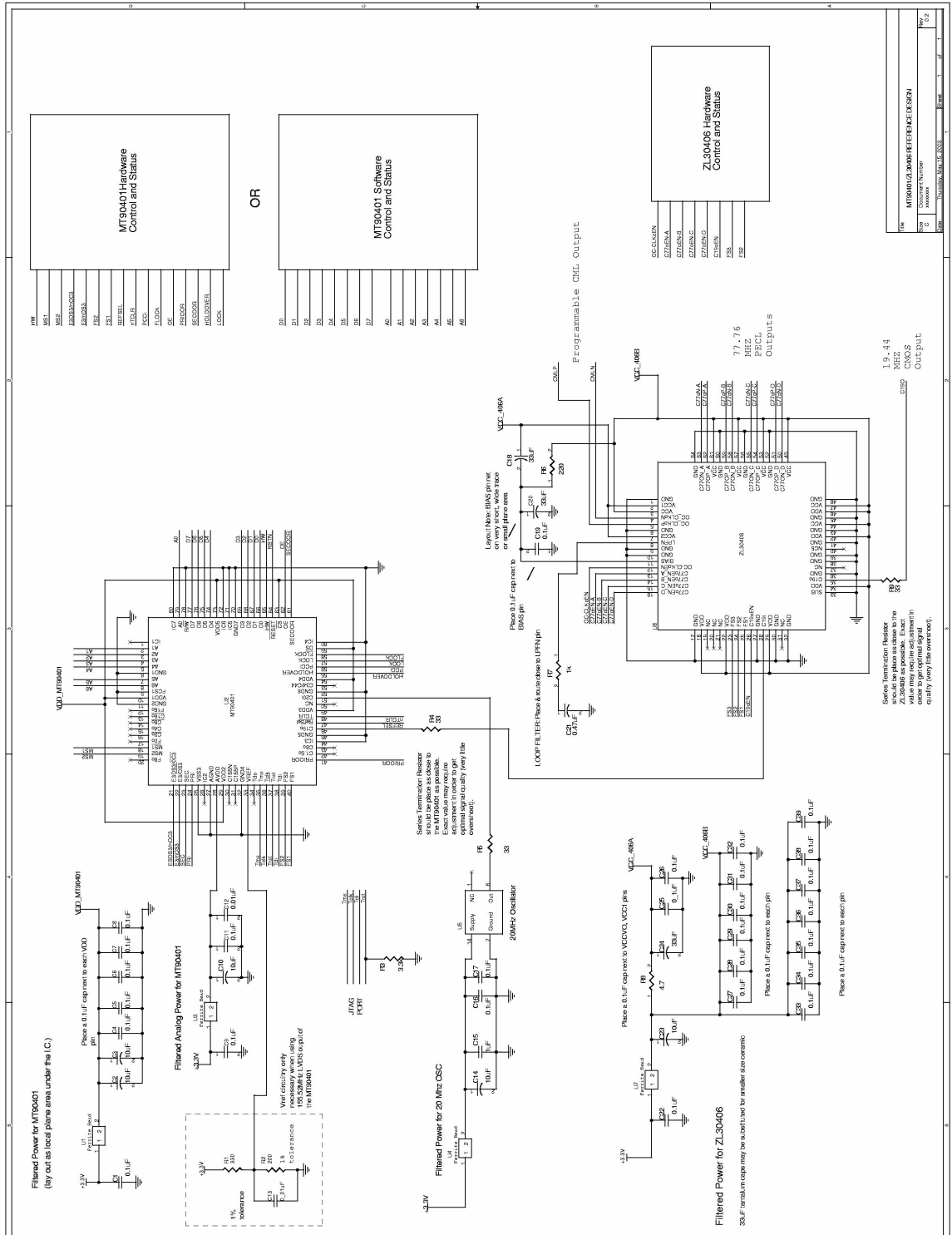



**For more information about all Zarlink products
visit our Web Site at
www.zarlink.com**

Information relating to products and services furnished herein by Zarlink Semiconductor Inc. or its subsidiaries (collectively "Zarlink") is believed to be reliable. However, Zarlink assumes no liability for errors that may appear in this publication, or for liability otherwise arising from the application or use of any such information, product or service or for any infringement of patents or other intellectual property rights owned by third parties which may result from such application or use. Neither the supply of such information or purchase of product or service conveys any license, either express or implied, under patents or other intellectual property rights owned by Zarlink or licensed from third parties by Zarlink, whatsoever. Purchasers of products are also hereby notified that the use of product in certain ways or in combination with Zarlink, or non-Zarlink furnished goods or services may infringe patents or other intellectual property rights owned by Zarlink.

This publication is issued to provide information only and (unless agreed by Zarlink in writing) may not be used, applied or reproduced for any purpose nor form part of any order or contract nor to be regarded as a representation relating to the products or services concerned. The products, their specifications, services and other information appearing in this publication are subject to change by Zarlink without notice. No warranty or guarantee express or implied is made regarding the capability, performance or suitability of any product or service. Information concerning possible methods of use is provided as a guide only and does not constitute any guarantee that such methods of use will be satisfactory in a specific piece of equipment. It is the user's responsibility to fully determine the performance and suitability of any equipment using such information and to ensure that any publication or data used is up to date and has not been superseded. Manufacturing does not necessarily include testing of all functions or parameters. These products are not suitable for use in any medical products whose failure to perform may result in significant injury or death to the user. All products and materials are sold and services provided subject to Zarlink's conditions of sale which are available on request.

Purchase of Zarlink's I²C components conveys a licence under the Philips I²C Patent rights to use these components in and I²C System, provided that the system conforms to the I²C Standard Specification as defined by Philips.

Zarlink, ZL and the Zarlink Semiconductor logo are trademarks of Zarlink Semiconductor Inc.

Copyright Zarlink Semiconductor Inc. All Rights Reserved.

TECHNICAL DOCUMENTATION - NOT FOR RESALE
