
ZL30151, ZL30169, ZL3025x, ZL30281, ZL30622, and ZL30722 Series Recommended Power Supply Decoupling and Layout Practices

Introduction

This document details the recommended power supply decoupling and layout practices for the ZL30151, ZL30169, ZL30250, ZL30251, ZL30252, ZL30253, ZL30622, and ZL30722 series of any-to-any clock multipliers, jitter attenuators, and telecom timing integrated circuits (ICs). This document also applies to the ZL30281 Three Output PCIe Clock Generator.

Power Supply Decoupling and Layout Practices

The following common design practices are recommended for improving device power supply noise rejection.

- Allocate one low-ESR 0.1 μF to 1 μF decoupling capacitor for each power pin. Example recommended capacitor types are ceramic X5R and X7R. Each capacitor should be located as close as possible to its respective device power pin. Each capacitor should be connected directly to the power pin and should not share vias to power or ground planes with other decoupling capacitors. Adjacent power pins 12 and 13 can share a single decoupling capacitor to reduce component count.
- Allocate one low-ESR 10 μF bulk capacitor for each device power domain. The power domains consist of the device's 1.8 V and 3.3V power supplies and any optional power islands used with the device's analog supplies. Example recommended capacitor types are ceramic X5R and X7R. Tantalum capacitors can also be used. These capacitors filter low frequency noise (up to several hundred kHz) that originates from switching power supplies. If a ferrite bead is used to connect a power island to a main board power plane, the associated bulk capacitor should be located close to the ferrite bead. Bulk decoupling capacitors can be shared with nearby devices powered by common power domains to reduce component count.
- Allocate one low-ESR 100 μF capacitor to pin VDDX033 when using a crystal resonator reference connected to pins XA and XB. Example recommended capacitor types are ceramic X5R and X7R. Tantalum capacitors can also be used.
- Connect the device's exposed ground pad (E-PAD) directly to the board's ground plane through a 4x4 array of vias spaced evenly across the pad.
- Power islands can be optionally used on the device's analog supplies to provide improved power rail noise rejection. A power island is a local copper area, separated from the main power plane by a series passive component such as a ferrite bead or low ohm resistor. When a ferrite bead is used, it should have a resistance of several hundred Ohms at 100 MHz. Additionally, it should have a current rating at least double the maximum current required by the associated device power pins to avoid core saturation and degraded performance. Finally, the combination of the ferrite bead inductance and supply decoupling capacitance should be chosen to avoid creating a resonant frequency which could cause gain peaking of a board noise source such as a switching power supply. For both the ferrite bead and low ohm resistor options, the voltage drop across this component must be taken into account in the board's power supply design to ensure the device's power rail specifications are met.

- Each of the ZL30151/169/250/251/252/253/281/622/722 output clocks has an independent power pin for signal format flexibility: VDDO1 for OC1, VDDO2 for OC2, and VDDO3 for OC3. When implementing the above guidelines, any output clock requiring a 3.3 V or 1.8 V supply can share a power island with the corresponding device core analog supply voltage to reduce component count. Additionally, output clock supplies of the same voltage can share a power island.

Figure 1 shows the application of these guidelines to a design which has all output clock signals configured as current-mode logic (CML) which requires a 3.3 V supply.

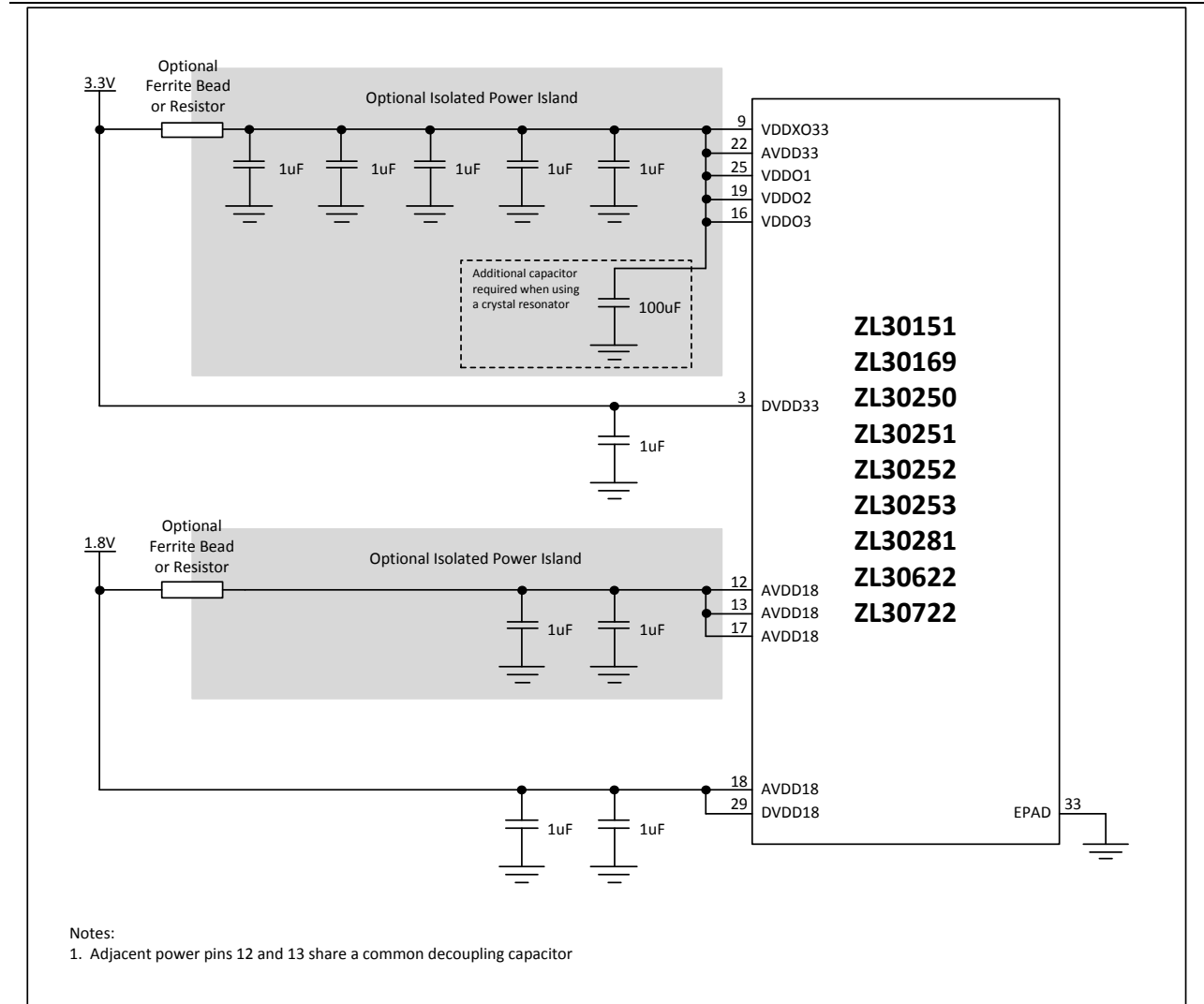


Figure 1 Example ZL30151/169/250/251/252/253/281/622/722 Power Supply Decoupling Scheme



Microsemi Corporate Headquarters
One Enterprise, Aliso Viejo,
CA 92656 USA

Within the USA: +1 (800) 713-4113
Outside the USA: +1 (949) 380-6100
Sales: +1 (949) 380-6136
Fax: +1 (949) 215-4996

E-mail: sales.support@microsemi.com

© 2017 Microsemi Corporation. All rights reserved. Microsemi and the Microsemi logo are trademarks of Microsemi Corporation. All other trademarks and service marks are the property of their respective owners.

Microsemi Corporation (Nasdaq: MSCC) offers a comprehensive portfolio of semiconductor and system solutions for communications, defense & security, aerospace and industrial markets. Products include high-performance and radiation-hardened analog mixed-signal integrated circuits, FPGAs, SoCs and ASICs; power management products; timing and synchronization devices and precise time solutions, setting the world's standard for time; voice processing devices; RF solutions; discrete components; security technologies and scalable anti-tamper products; Power-over-Ethernet ICs and midspans; as well as custom design capabilities and services. Microsemi is headquartered in Aliso Viejo, Calif., and has approximately 3,400 employees globally. Learn more at www.microsemi.com.

Microsemi makes no warranty, representation, or guarantee regarding the information contained herein or the suitability of its products and services for any particular purpose, nor does Microsemi assume any liability whatsoever arising out of the application or use of any product or circuit. The products sold hereunder and any other products sold by Microsemi have been subject to limited testing and should not be used in conjunction with mission-critical equipment or applications. Any performance specifications are believed to be reliable but are not verified, and Buyer must conduct and complete all performance and other testing of the products, alone and together with, or installed in, any end-products. Buyer shall not rely on any data and performance specifications or parameters provided by Microsemi. It is the Buyer's responsibility to independently determine suitability of any products and to test and verify the same. The information provided by Microsemi hereunder is provided "as is, where is" and with all faults, and the entire risk associated with such information is entirely with the Buyer. Microsemi does not grant, explicitly or implicitly, to any party any patent rights, licenses, or any other IP rights, whether with regard to such information itself or anything described by such information. Information provided in this document is proprietary to Microsemi, and Microsemi reserves the right to make any changes to the information in this document or to any products and services at any time without notice.