

---


## AN02 Microsemi MMIC Amplifiers with On-Chip Power Detectors

---

Microsemi® designs and manufactures GaAs MMIC amplifiers, many of which have an on-chip differential diode power detector. This feature can be used with an external op-amp circuit, or a microprocessor with a lookup table, to enable real time output power detection.

### Output power detector basics

The block diagram of the on-chip power detector is shown in *Figure 1*. The circuitry consists of two diodes, one with an RF signal and DC offset ( $V_{RF}$ ) and the other with only a DC offset ( $V_{DC}$ ). This topology allows for common mode cancellation of diode temperature drift and good log linearity versus power

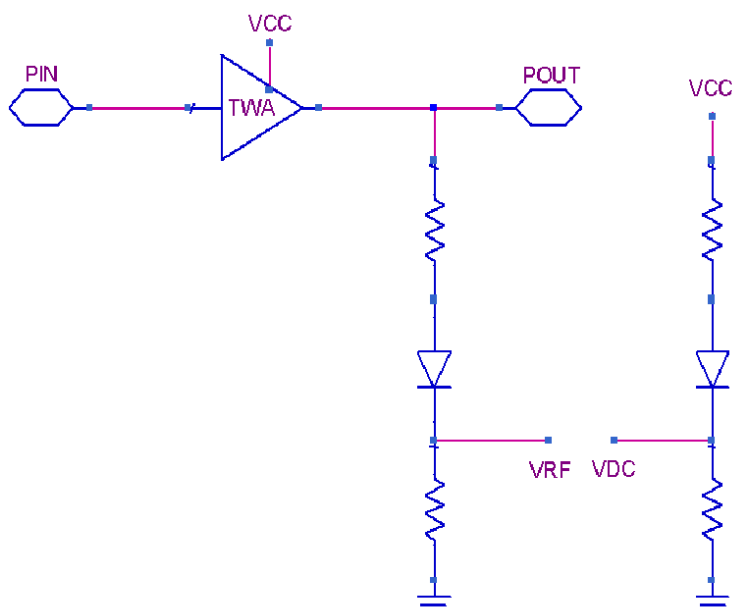


**Figure 1. Simplified on-chip power detector**

Most Microsemi MMIC amplifiers feature this power detector, but since the nominal DC bias of each amplifier varies, the DC offset voltage will be slightly different from family to family.

This application note details the power detector on the Microsemi MMA034AA, a 0.04-65GHz GaAs MMIC amplifier nominally biased with 8V, 250mA. However, the circuits recommended in this application note will work for all Microsemi TWA amplifiers.

## Measurements of the power detector


Differential measurements of the MMA034AA power detector are shown in *Figure 2*. The graph shows the detector voltage ( $V_{RF}$ ) with the reference voltage ( $V_{DC}$ ) removed ( $V_{RF} - V_{DC}$ ), which effectively eliminates the common mode diode temperature drift from the measurement. The difference voltage is plotted at frequencies from 2-40GHz, swept across a range of output power levels.

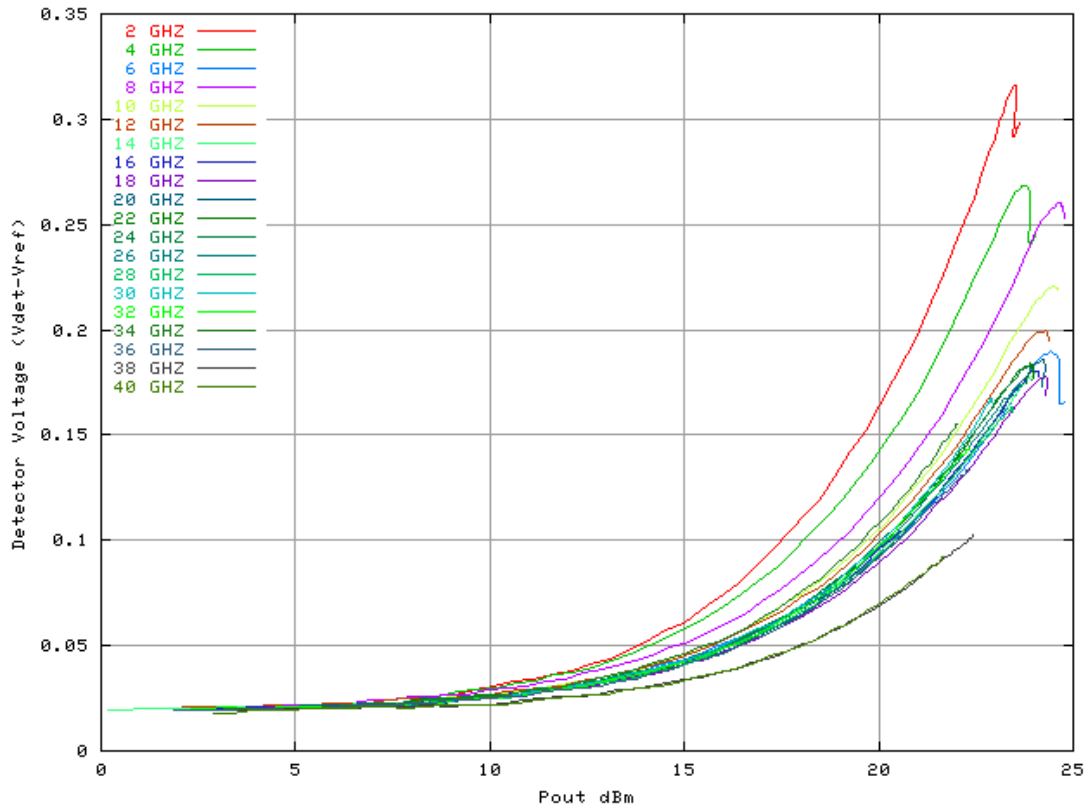

**Figure 2. Differential detector output (logarithmic)**

Note the 0.02V DC offset on the measurement. The DC offset can be removed with the same op-amp circuit that is used to generate the difference voltage, shown in *Figure 4*.

The detector output shows good log linearity, as shown in *Figure 3*.

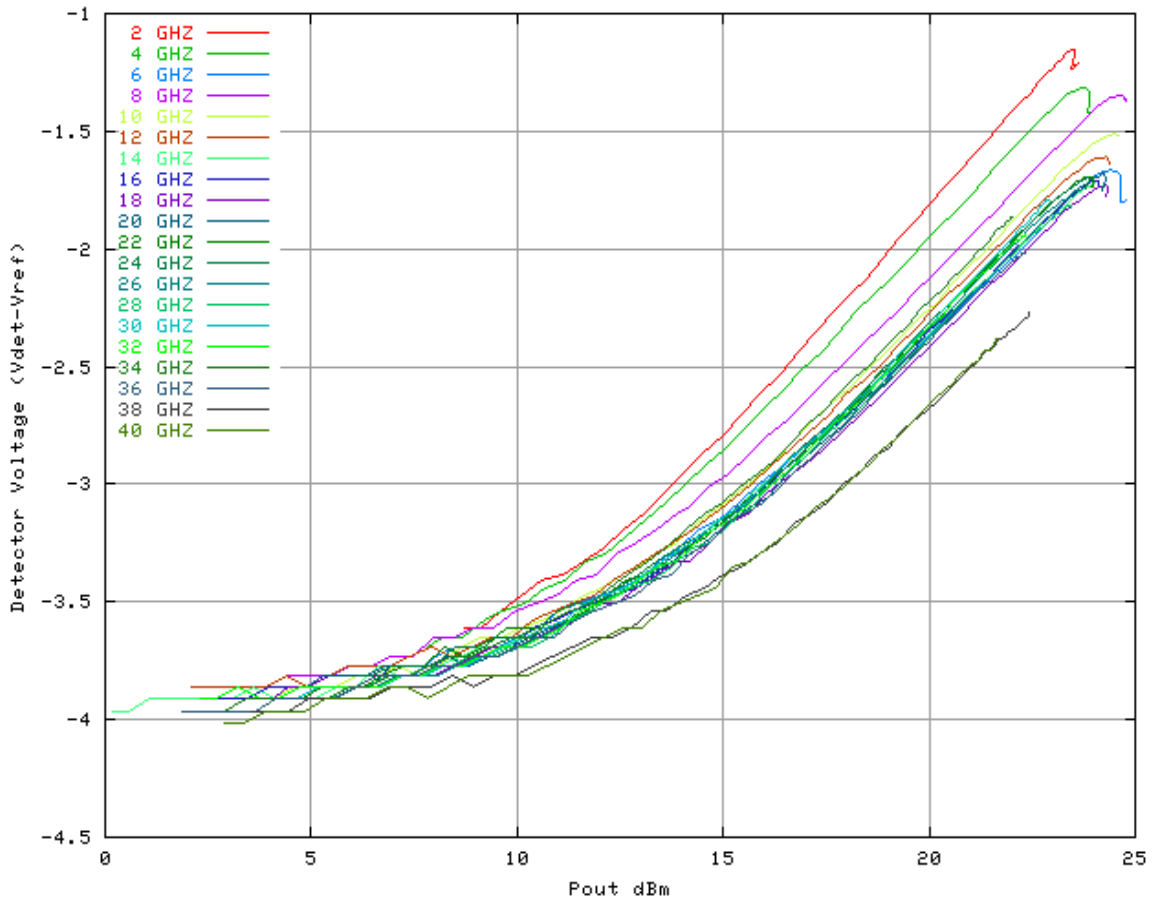


**Figure 3. Differential detector output (logarithmic)**

However, much improved log linearity can be achieved by removing the DC offset from the difference voltage, as discussed in the next section. Removing the small DC offset enables the full dynamic range of the detector.

### Power detector measurements with offset adjustment

To obtain the full dynamic range of the device, the DC offset voltage must be removed from the difference voltage. This improves the low power noise floor and the log linearity as shown in *Figure 6*.

An example opamp circuit to determine the difference voltage, with DC offset removed, is shown in *Figure 4*; this circuit is designed for unity gain (the 50k $\Omega$  feedback resistor can be increased for higher voltage output).

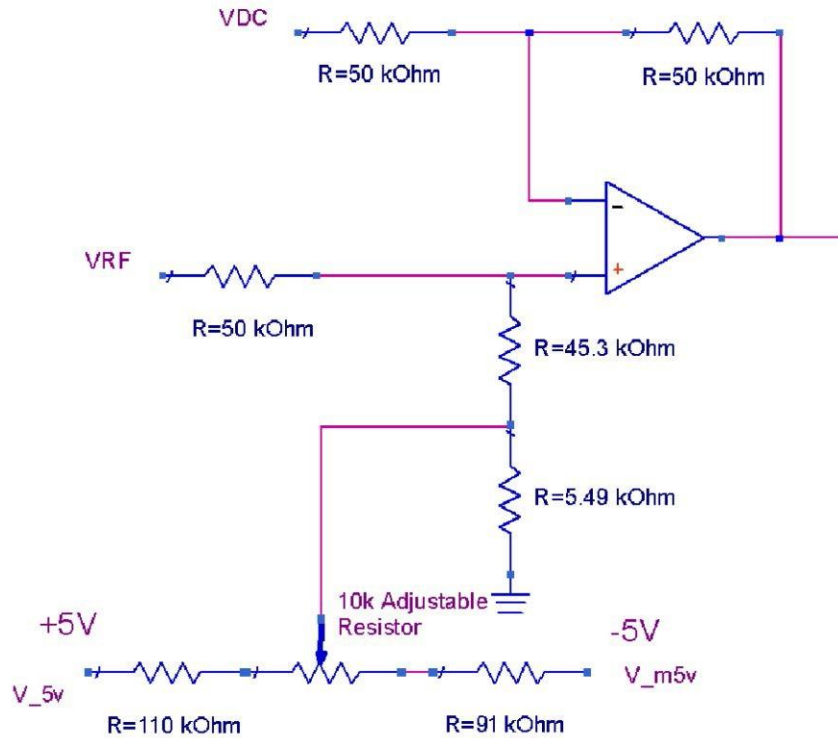


**Figure 4. Op-amp circuit to remove the DC offset voltage**


The DC offset can be removed by adjusting the 10k $\Omega$  resistor in the divider network connected to the  $V_{RF}$  op-amp input.

Removing the DC offset decreases the lower range of the detector from +13dBm to +5dBm, illustrated by comparing *Figure 3* and *Figure 6*. This effectively increases the dynamic range of the power detector by 8dB.

*Figure 5* shows the linear output voltage with the DC offset removed as per the op-amp circuit shown above. *Figure 6* shows the same corrected output voltage plotted on a logarithmic scale. The linearity is excellent from +5dBm to the maximum range of the detector.

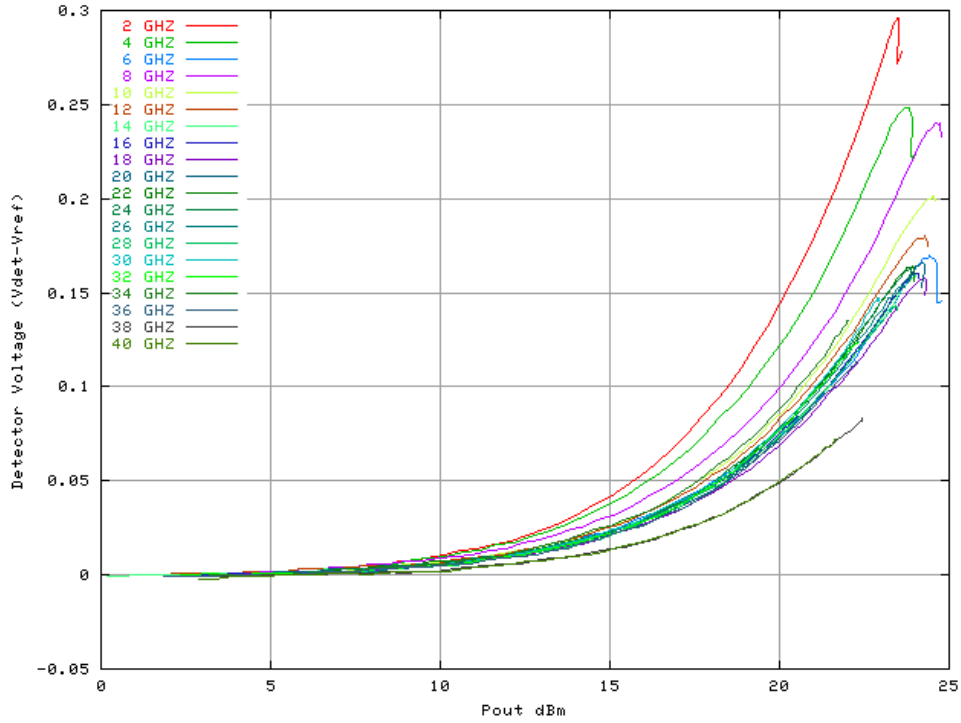


**Figure 5. Offset-removed detector output (linear)**

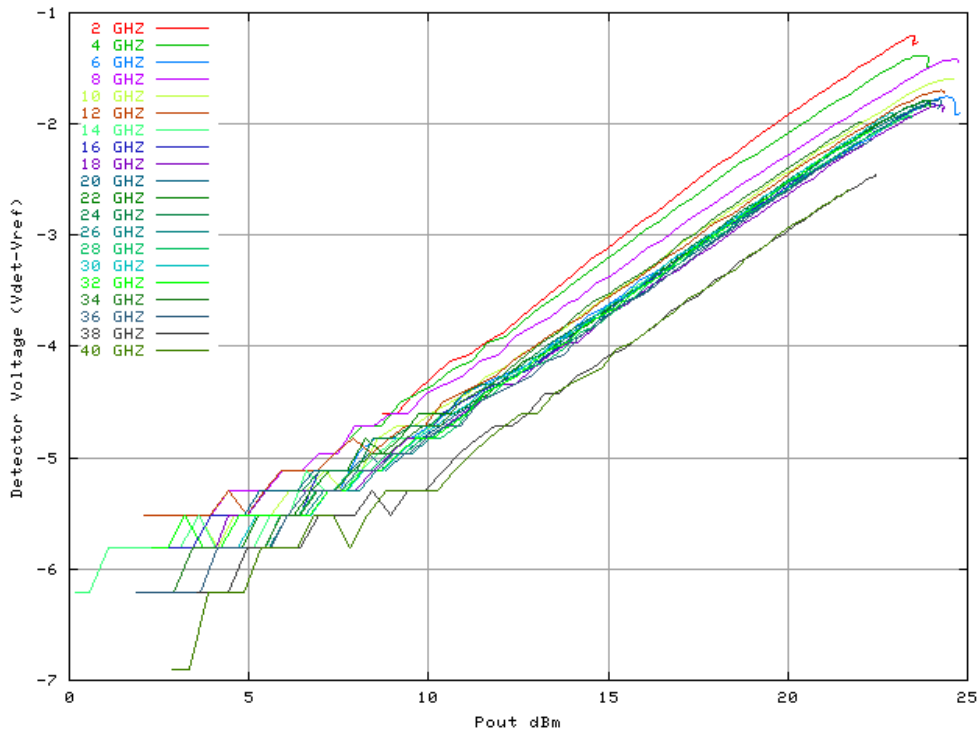

**Figure 6. Offset-removed detector output (logarithmic)**

The power detector difference voltage is also very stable across a wide temperature range, as shown in *Figure 7*.

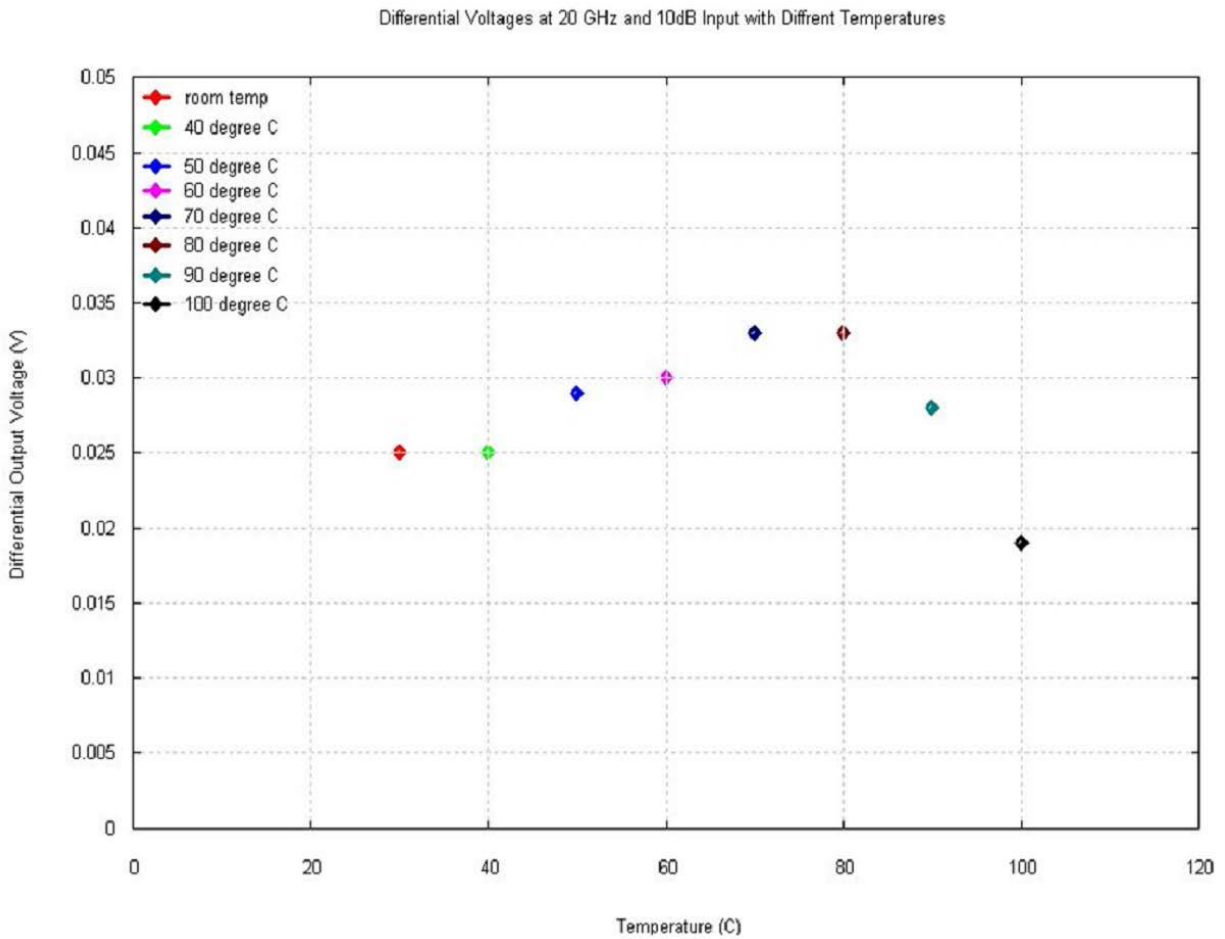

**Figure 7. Op-amp circuit to remove the DC offset voltage**



**Microsemi Corporate Headquarters**  
One Enterprise, Aliso Viejo CA 92656 USA  
Within the USA: +1 (800) 713-4113  
Outside the USA: +1 (949) 380-6100  
Sales: +1 (949) 380-6136  
Fax: +1 (949) 215-4996  
E-mail: [sales.support@microsemi.com](mailto:sales.support@microsemi.com)

Microsemi Corporation (Nasdaq: MSCC) offers a comprehensive portfolio of semiconductor and system solutions for communications, defense and security, aerospace, and industrial markets. Products include high-performance and radiation-hardened analog mixed-signal integrated circuits, FPGAs, SoCs, and ASICs; power management products; timing and synchronization devices and precise time solutions, setting the world's standard for time; voice processing devices; RF solutions; discrete components; security technologies and scalable anti-tamper products; Power-over-Ethernet ICs and midspans; as well as custom design capabilities and services. Microsemi is headquartered in Aliso Viejo, Calif. and has approximately 3,400 employees globally. Learn more at [www.microsemi.com](http://www.microsemi.com).

---

© 2014 Microsemi Corporation. All rights reserved. Microsemi and the Microsemi logo are trademarks of Microsemi Corporation. All other trademarks and service marks are the property of their respective owners.