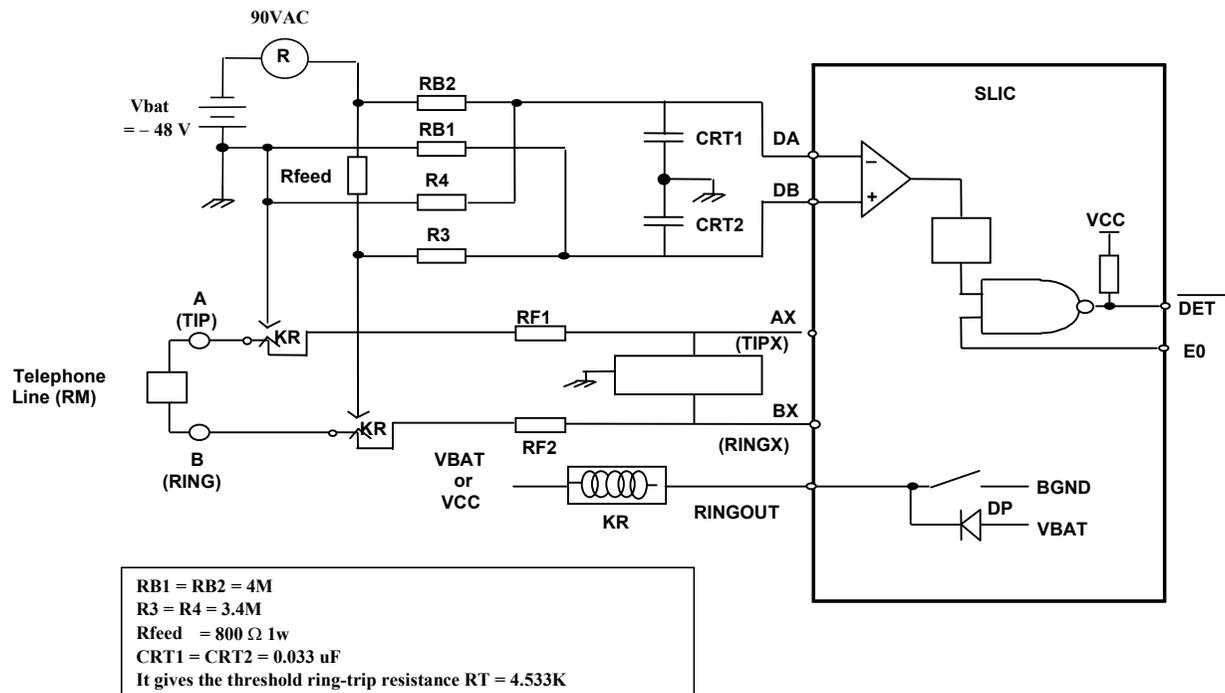


**APPLICATION NOTE**

Several of Zarlink's SLIC products offer DA/DB pins that allow external input signals to be applied to the SLIC. These pins allow the user to connect to off-board custom-built ringing circuitry.

An example of the type of circuitry recommended is similar to what is shown in Figure 1.

**Figure 1. External Ringing Circuitry**


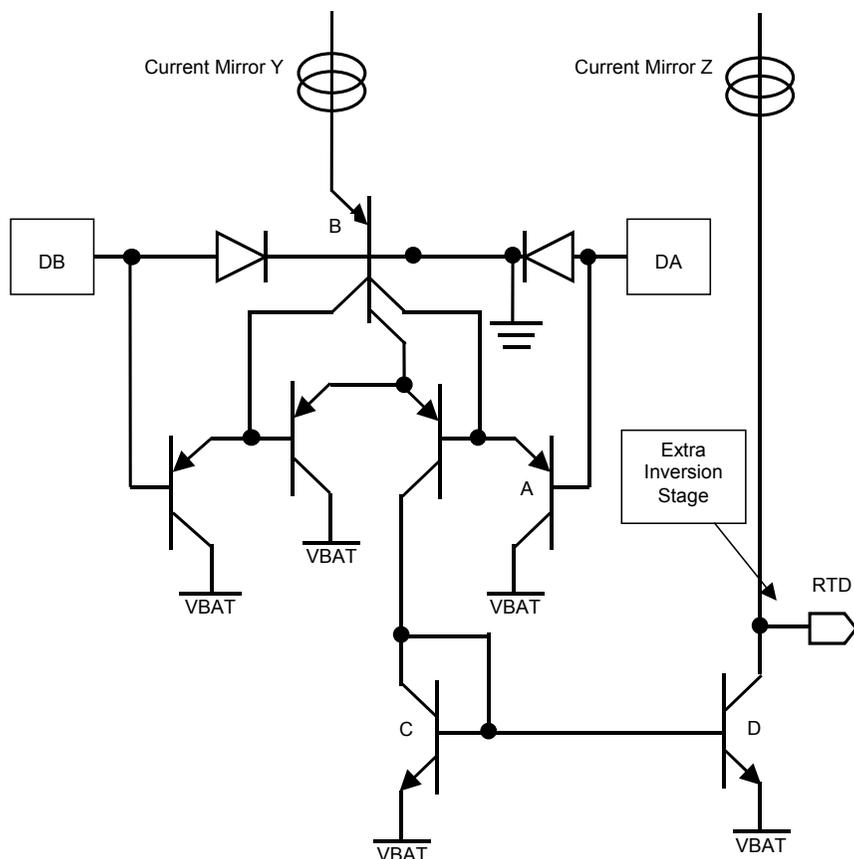
This allows operation in half-battery, with a DA/DB delta of  $-1.8 \text{ V}$  when on-hook.

There are two different internal SLIC configurations of the DA/DB circuitry. These are functionally equivalent when used in a standard application. However, if the ring-trip comparator is used in a different way, different behavior is seen if the voltages at DA and DB operate very close to BGND. The following describes each circuit and the resulting behavior when operating these inputs near to ground.

The following circuitry applies to these devices:

Am7942, Am7943, Am7944, Am7945, Am7946, Am79467, Am79467-X, Am7947, Am7949, Am795xx, and the Am79M5xx.

Figure 2. DA/DB Circuitry Internal to SLIC (Newer) Devices



The way this circuit operates is:

**During a non-tripped mode:**

1. DB is less than DA.
2. The voltage on DB turns on the DB half of this comparator.
3. This forces all the current going through transistor B into transistors A and C.
4. The current mirror formed by transistors C-D shunts all the current from current mirror Z away from "RTD", preventing a detect signal from occurring.

**During a tripped mode:**

1. DA is less than DB.
2. The voltage on DA turns on the DA half of this comparator (stealing the current from the DB half).
3. This forces all the current going away from transistors A and C.
4. The current mirror formed by transistors C-D turns "off" and all of the current from current mirror Z goes into "RTD" and generates a detect signal.

**Typical Voltage required on DB for circuit to operate at temp = 25°C:**


$$DB < -(V_{SAT} \text{ of transistor B}) - (V_{BE} \text{ of Transistor A}) \cong -(0.20 \text{ V}) - (0.60 \text{ V}) \cong -0.8 \text{ V}$$

⇒ Assume -1.00 V with margin for internal IR drops.

The following circuitry applies to these optimized designs:

Am7920, Am7922, Am7924, Am79485, and the Am79489.

Figure 3. DA/DB Circuitry Internal to SLIC (Optimized) Devices

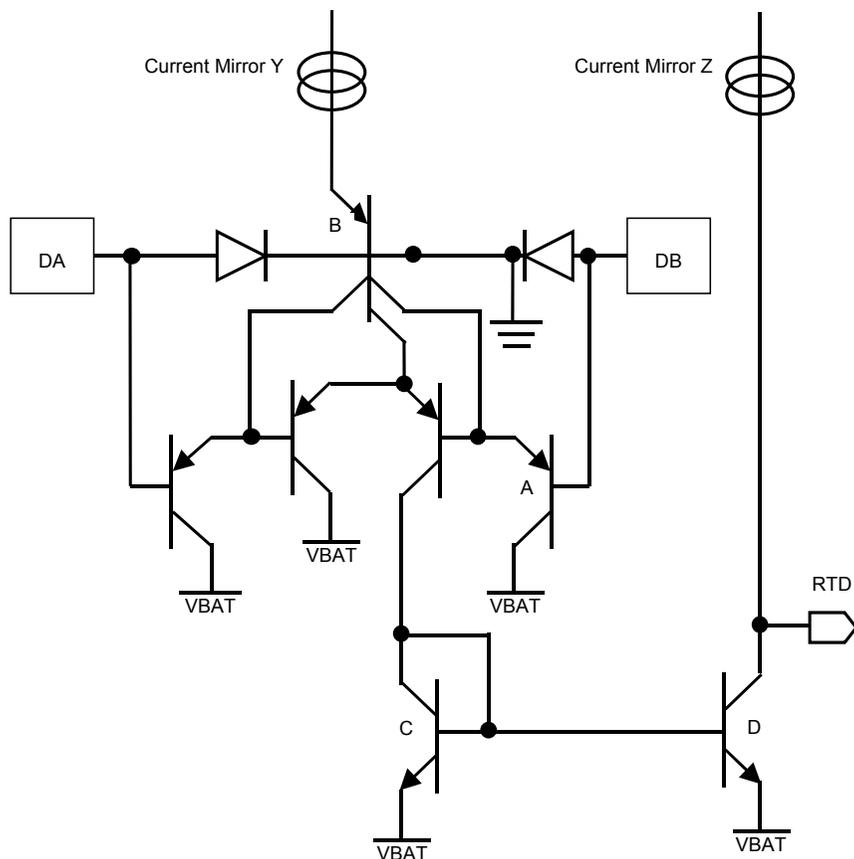

### Circuit Operation if DB Does Not Have a Sufficient Negative Voltage

In Figure 3, when DB moves too close to ground, then the DB half of the comparator turns off independent of the voltage on DA. This results in no current flowing in transistor C and the device appearing to ring trip as transistor D is no longer able to shunt the current from mirror Z to ground. The voltage on DA will not affect this behavior. Therefore, these inputs should be operated between  $-1.25\text{ V}$  and VBAT potential.

The design shown in Figure 2 is less efficient, and produces different behavior when DA and/or DB are close to ground. In these designs, an extra inversion stage was used on the RTD signal, and DA and DB were swapped to obtain the desired operational behavior. This does not change the circuit operation when DA and DB are operating at their typical voltages (near  $\text{VBAT}/2$ ), but does affect operation when DA and DB are operating very near to ground. With this configuration, if DB is held near to ground, then this leg of the comparator turns off. However, if DA is still more positive than DB (true if the inputs are indicating 'ON HOOK'), then both halves of the comparator are off. There is no current flow in transistors C and D. In this case, there is a further inversion, which means that the SLIC still indicates 'ON HOOK'. From this point, if DA swings sufficiently negative, then transistor A turns on, producing current flow in C, which will produce an 'OFF HOOK' indication, which is the desired result. However, under these conditions, the offset between DB and DA increases, and in reality the turn-on point for DA is now independent of DB.

Even with this design, the same operating range of  $-1.25\text{ V}$  to VBAT is recommended for DA and DB to ensure correct comparator operation.



**For more information about all Zarlink products  
visit our Web Site at  
[www.zarlink.com](http://www.zarlink.com)**

Information relating to products and services furnished herein by Zarlink Semiconductor Inc. or its subsidiaries (collectively "Zarlink") is believed to be reliable. However, Zarlink assumes no liability for errors that may appear in this publication, or for liability otherwise arising from the application or use of any such information, product or service or for any infringement of patents or other intellectual property rights owned by third parties which may result from such application or use. Neither the supply of such information or purchase of product or service conveys any license, either express or implied, under patents or other intellectual property rights owned by Zarlink or licensed from third parties by Zarlink, whatsoever. Purchasers of products are also hereby notified that the use of product in certain ways or in combination with Zarlink, or non-Zarlink furnished goods or services may infringe patents or other intellectual property rights owned by Zarlink.

This publication is issued to provide information only and (unless agreed by Zarlink in writing) may not be used, applied or reproduced for any purpose nor form part of any order or contract nor to be regarded as a representation relating to the products or services concerned. The products, their specifications, services and other information appearing in this publication are subject to change by Zarlink without notice. No warranty or guarantee express or implied is made regarding the capability, performance or suitability of any product or service. Information concerning possible methods of use is provided as a guide only and does not constitute any guarantee that such methods of use will be satisfactory in a specific piece of equipment. It is the user's responsibility to fully determine the performance and suitability of any equipment using such information and to ensure that any publication or data used is up to date and has not been superseded. Manufacturing does not necessarily include testing of all functions or parameters. These products are not suitable for use in any medical products whose failure to perform may result in significant injury or death to the user. All products and materials are sold and services provided subject to Zarlink's conditions of sale which are available on request.

Purchase of Zarlink's I2C components conveys a license under the Philips I2C Patent rights to use these components in an I2C System, provided that the system conforms to the I2C Standard Specification as defined by Philips.

Zarlink, ZL, the Zarlink Semiconductor logo and the Legerity logo and combinations thereof, VoiceEdge, VoicePort, SLAC, ISLIC, ISLAC and VoicePath are trademarks of Zarlink Semiconductor Inc.

**TECHNICAL DOCUMENTATION - NOT FOR RESALE**

---