

# FETs Enhance Switched-Mode Designs

## Abstract

Switched-mode power supplies are well known for their high levels of efficiency and for their compactness. Further improvements can be effected by employing power MOSFETs in place of conventional bipolar transistors. A practical design for a 5 V, 20 A supply is suggested utilizing the SG1526.


Many of the basic design concepts relating to power MOSFETs were outlined in an earlier article "Designing with power MOSFETs," which was published in the March, 1982 issue of *Electronic Product Design*. Now let us apply some of the driver techniques discussed in the earlier article, to a 100 kHz, 100 W switched-mode power supply. Fig. 1 shows the circuit which is truly universal in that it operates directly from a mains voltage spanning 85 V to 265 V r.m.s. without any mechanical switching requirements. And further-more, it is able to perform this task over a wide frequency spread, typically from 50 Hz to 400 Hz.

### SIMPLICITY OF DESIGN

At the centre of the design is a 500 V, 3 A power MOSFET (Q1) which converts the rectified mains voltage into a tightly controlled 100 W d.c. output. Apart from the indicated rectifiers and Zener diodes, the power FET and its regulating pulse-width modulated driver IC (SG1526) are the only active devices needed to achieve a full-load efficiency of 74% with  $\pm 0.5\%$  regulation. This particular design has a maximum output current of 20 A d.c. at 5 V with a maximum ripple of 50 mV pk. -pk. Transient response for a step change of 10 A load current is 500 mV, settling within 250  $\mu$ s.

### MORE EFFICIENT

For a given combination of voltage and current ratings, power MOSFETs can generally switch more efficiently and at much higher frequencies than their bipolar counterparts. Because power MOSFETs can be operated at higher frequencies, smaller transformers and filter capacitors can be used leading to more compact designs. The circuit shown in Fig. 1, for example, operates at 100 kHz, some two and a half times faster than most circuits using bipolar transistors.

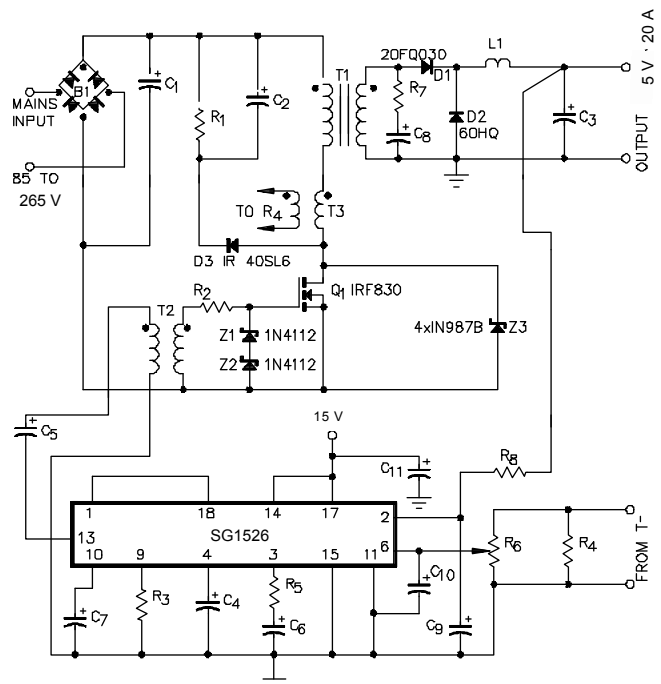

**Figure 1.** Versatile 100 W Switched-Mode Power Supply Offers 20 A Output with 75 Percent Efficiency and a Tight Performance Spec.; See Text for Details.

The higher operating frequency also enables the circuit to recover much more quickly from severe line or load variations. This is especially important in situations where a system's power-up signal is used to reset a large number of logic devices simultaneously.

Driving a power MOSFET is in most cases much easier than driving an equivalent bipolar device, it being voltage rather than current driven. Some gate drive is of course required, but at a much lower level than that associated with similarly rated bipolar devices.

## MODIFICATIONS

The power MOSFET is not directly compatible with the bipolar power transistor and cannot be used in a switched mode circuit without modification.


Irrespective of the power switching device used, be it a MOSFET or a bipolar power transistor, the associated pulse-width modulated switcher cannot normally be left on for more than 50% of the total duty cycle. Under normal circumstances, a 50% on time occurs only when the input voltage is very low and the output current is high. Conversely, the shortest on times occur when the input voltage is near to its peak and the output current is minimal.

Ideally, the pulse-width modulator should operate over a very wide duty cycle range to ensure close regulation with wide line and load extremes. Unfortunately, it has been impracticable to implement this approach in bipolar designs, since the gain of bipolar transistors decreases rapidly when operated in the short-pulse, high-current mode.

A power MOSFET's transconductance, on the other hand, does not vary so widely with current changes. This makes it much easier to drive a MOSFET directly, using a short duty cycle. Furthermore, the short conduction time at high input voltage leaves a relatively long time to reset the associated transformer and thus reduce the peak voltage across the MOSFET. Also the designer is able to use 500 V rated devices in mains driven supplies in contrast to the usual 800 V rating often needed for circuits featuring bipolar devices.

## PROTECTION

Some protection is of course necessary. The MOSFET shown in Fig. 1, for example, features clamping diodes (Zener diodes 1 and 2) to limit the circuit's maximum gate voltage to 18 V. Zener 3 which comprises four series-connected 120 V diodes, restricts the source/drain swing to 450 V to give a safe working margin.

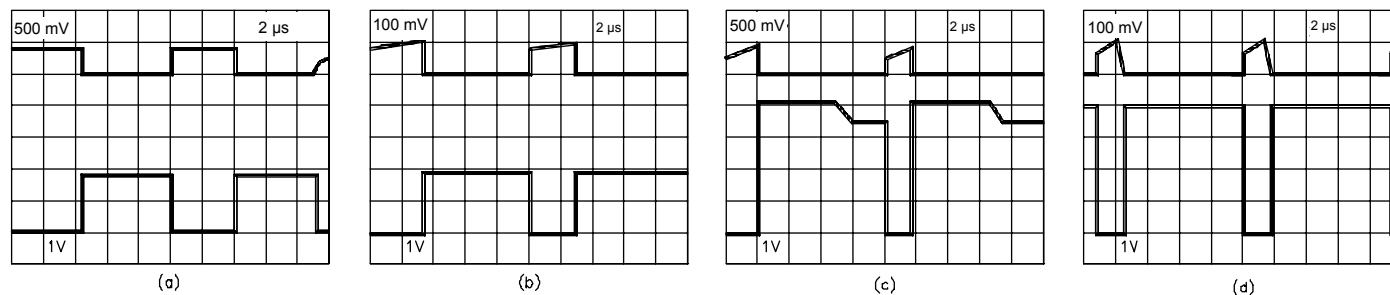


**Figure 2.** Switching Waveforms. With an 85 V Line and a 20 A Load (a) Shows Drawn Current on the Upper Trace and Drain Voltage on the Lower. The Load is Cut to 5 A in (b), While (c) and (d) Show the Same Parameters at a 265 V Line Voltage with Respective Loads of 20 A and 5 A.

The resistor/capacitor/diode snubber formed by R1/C2/D3 conforms in the principle to the approach outlined in the earlier article, except that it is allowed to float. For more details on this and other related topics, refer to International Rectifier's application note AN-939.

Trials have shown that worst-case efficiency occurs at virtually maximum input voltage with minimum loading. Here efficiency drops to just under 70 percent, compared with 76 percent at maximum output. Dissipation is thus around 8 W at maximum output and slightly higher than this value when the supply is lightly loaded.


## OPERATION

The off-screen photographs show how the circuit functions. Fig. 2 demonstrates how the pulse-width modulator controls the MOSFET's conduction time with respect to various load and line conditions. At one extreme, the input voltage is down to 85 V, while output is at 20 A. Fig. 2a shows the MOSFET on for 4  $\mu$ s which gives a duty cycle of approximately 44 percent. When operating at the other extreme, i.e. 265 V input and 5 A output, the MOSFET is on for approximately 1  $\mu$ s, which corresponds to a 10 percent duty cycle. Note how the gate/source waveforms which are depicted in Fig. 3 relate to the operating levels shown in Fig. 2.

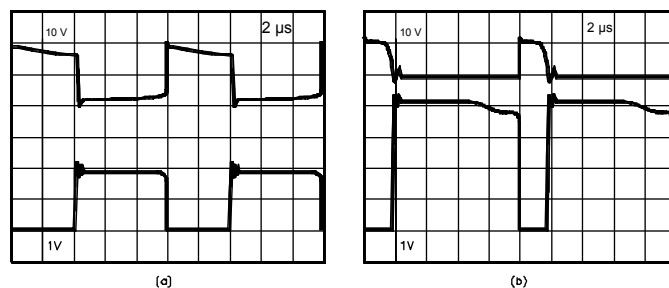

**Figure 3.** Gate/Source Waveforms. These Were Recorded with the Unit Under Full Load, (a) with a Line Voltage of 85 V and (b) with a Line Voltage of 265 V. The Upper Traces Show Gate/Source Voltage While the Lower Show Drain Voltage.

Typical voltage waveforms across the output rectifiers are shown in Fig. 4. Note that while the forward rectifier D1 blocks a peak voltage (including the commutation transient) of about 12 V, D2 has to withstand around 75 V for a 5 V output, due to the short conduction cycle. Both of these diodes contribute to the system's net losses. Indeed, these devices dissipate some 30 to 50 percent of the switching energy, and represent a major problem in designing low output voltage power supplies. Losses from the rectifier diodes are approximately the same for both the 5 V and 15 V supply designs.

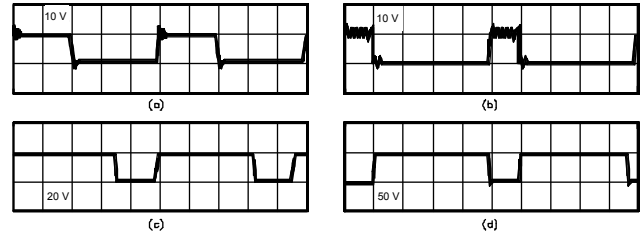

TRACE	PARAMETER	CONDITIONS	VERTICAL	HORIZONTAL
a	D1 VOLTAGE	35 V LINE	10 V/DIV	2 $\mu$ s/DIV
b	D2 VOLTAGE	5 A LOAD	20 V/DIV	
c	D1 VOLTAGE	265 V LINE	20 V/DIV	50 V/DIV
d	D2 VOLTAGE	5 A LOAD	50 V/DIV	

**Figure 4.** Output circuit waveforms. The Upper Traces show the voltage waveform appearing across D1, while the Lower covers rectifier D2. In both cases load is at 5 A;(a) with the input voltage at 85 V and (b) at 265 V.



**Microsemi Corporate Headquarters**  
One Enterprise, Aliso Viejo,  
CA 92656 USA

**Within the USA:** +1 (800) 713-4113  
**Outside the USA:** +1 (949) 380-6100  
**Sales:** +1 (949) 380-6136  
**Fax:** +1 (949) 215-4996

**E-mail:** [sales.support@microsemi.com](mailto:sales.support@microsemi.com)

© 2015 Microsemi Corporation. All rights reserved. Microsemi and the Microsemi logo are trademarks of Microsemi Corporation. All other trademarks and service marks are the property of their respective owners.

Microsemi Corporation (Nasdaq: MSCC) offers a comprehensive portfolio of semiconductor and system solutions for communications, defense & security, aerospace and industrial markets. Products include high-performance and radiation-hardened analog mixed-signal integrated circuits, FPGAs, SoCs and ASICs; power management products; timing and synchronization devices and precise time solutions, setting the world's standard for time; voice processing devices; RF solutions; discrete components; security technologies and scalable anti-tamper products; Ethernet solutions; Power-over-Ethernet ICs and midspans; as well as custom design capabilities and services. Microsemi is headquartered in Aliso Viejo, Calif., and has approximately 3,600 employees globally. Learn more at [www.microsemi.com](http://www.microsemi.com).

Microsemi makes no warranty, representation, or guarantee regarding the information contained herein or the suitability of its products and services for any particular purpose, nor does Microsemi assume any liability whatsoever arising out of the application or use of any product or circuit. The products sold hereunder and any other products sold by Microsemi have been subject to limited testing and should not be used in conjunction with mission-critical equipment or applications. Any performance specifications are believed to be reliable but are not verified, and Buyer must conduct and complete all performance and other testing of the products, alone and together with, or installed in, any end-products. Buyer shall not rely on any data and performance specifications or parameters provided by Microsemi. It is the Buyer's responsibility to independently determine suitability of any products and to test and verify the same. The information provided by Microsemi hereunder is provided "as is, where is" and with all faults, and the entire risk associated with such information is entirely with the Buyer. Microsemi does not grant, explicitly or implicitly, to any party any patent rights, licenses, or any other IP rights, whether with regard to such information itself or anything described by such information. Information provided in this document is proprietary to Microsemi, and Microsemi reserves the right to make any changes to the information in this document or to any products and services at any time without notice.